

DFCCIL

Previous Year Paper
Executive (Electrical)
11 Nov, 2018 Shift 2

Participant ID	
Participant Name	
Test Center Name	
Test Date	11/11/2018
Test Time	12:30 PM - 2:30 PM
Subject	Executive Electrical

Section : General Aptitude Knowledge

Q.1 In which state does the greatest number of Uranium mines exist as of September 2018?

- Ans ☒ 1. Jharkhand
- ☐ 2. Odisha
- ☐ 3. Madhya Pradesh
- ☐ 4. Chhattisgarh

Question ID : 1860451986
Status : Answered
Chosen Option : 1

Q.2 National Rail and Transport Institute, India's first railway university, has been opened in which of the following states?

- Ans ☐ 1. Telangana
- ☐ 2. Bihar
- ☒ 3. Gujarat
- ☐ 4. Uttar Pradesh

Question ID : 1860451992
Status : Answered
Chosen Option : 3

Q.3 विश्व अधिक मंच (2018) द्वारा जारी 74 उभरती अर्थव्यवस्थाओं के समावेशी विकास सूचकांक में भारत का स्थान कौन सा है?

- Ans ☐ 1. 42वाँ
- ☐ 2. 72वाँ
- ☒ 3. 62वाँ
- ☐ 4. 52वाँ

Question ID : 1860451993
Status : Answered
Chosen Option : 3

Q.4 मसौशिया में सितंबर 2018 में आयोजित एक सम्मेलन में, किस राज्य-पर्यटन को अपने अभिलेख निपणन अभियानों के लिए प्रशासक एशिया यात्रा एसोसिएशन (याटा) के दो प्रतिष्ठित स्वर्ण पुरस्कार प्रदान किये गए हैं?

- Ans ☐ 1. उत्तर प्रदेश
- ☒ 2. केरल
- ☐ 3. गोवा
- ☐ 4. पश्चिम बंगाल

Question ID : 1860451989
Status : Answered
Chosen Option : 3

Q.5 _____ of the Constitution of India deals with _____.

Ans

Question ID : 1860451997
Status : Answered

1. Article 40, fundamental duties

2. Article 45, uniform civil code

3.

Article 40, organisation of village panchayats

4. Article 48A, uniform civil code

Chosen Option : 3

Q.6 Which state is the largest producer of wind energy in India?

- Ans

1. Tamil Nadu

2. Maharashtra

3. Gujarat

4. Rajasthan

Question ID : 1860451987

Status : Answered

Chosen Option : 4

Q.7 In which state has the Government of India launched the first Tribal Circuit Project under the Swadesh Darshan Scheme?

- Ans

1. Jharkhand

2. Madhya Pradesh

3. Chhattisgarh

4. Bihar

Question ID : 1860451990

Status : Answered

Chosen Option : 3

Q.8 The ray that comes back from a surface after the reflection is known as _____.

- Ans

1. a reflected ray

2. an x-ray

3. an incident ray

4. an alpha ray

Question ID : 1860451995

Status : Answered

Chosen Option : 1

Q.9 Which Indian boxer won a Gold Medal in Asian Games 2018?

- Ans

1. Manoj Kumar

2. Amit Panghal

3. Gaurav Solanki

4. Shiva Thapa

Question ID : 1860451991

Status : Answered

Chosen Option : 2

Q.10 Which of the following is correct?

- Ans

1.

Sucheta Kriplani was the first woman Chief Minister of Uttar Pradesh.

2.

Nandini Satpathy was the first woman Chief Minister of Uttar Pradesh.

3.

Shashikala Kakodkar was the first woman Chief Minister of Uttar Pradesh.

4.

Janaki Ramachandran was the first woman Chief Minister of Uttar Pradesh.

Question ID : 1860451988

Status : Answered

Chosen Option : 1

Q.11 जब काँच की एक छड़ को रेशम पर रगड़ा जाता है, तो इसके द्वारा प्राप्त आवेश को परंपरागत रूप से क्या कहा जाता है?

- Ans

1. धनात्मक

Question ID : 1860451994

Status : Answered

- ☒ 2. ऋणात्मक
- ☒ 3. तटस्थ
- ☒ 4. प्राकृतिक

Chosen Option : 1

Q.12 After full moon day, the size of the bright part of the moon appears to become thinner and thinner every night. On the fifteenth day, the moon is not visible. This day is known as the:

- Ans**
- ☒ 1. New moon day
 - ☒ 2. Moon day
 - ☒ 3. Full moon day
 - ☒ 4. Half-moon day

Question ID : 1860451996

Status : Answered

Chosen Option : 1

Section : Logical Reasoning

Q.1 दी गई अक्षर श्रृंखला में, रिक्त स्थानों पर किस अक्षर समूह को क्रमिक रूप से रखा जाए, जिस से वह श्रृंखला को पूर्ण करेगा?

_qr_rp_pqp_r_rp

- Ans**
- ☒ 1. pqqrr
 - ☒ 2. pqrqq
 - ☒ 3. qqqr
 - ☒ 4. qppqp

Question ID : 1860451999

Status : Answered

Chosen Option : 2

Q.2

Question ID : 1860452009

Status : Answered

Chosen Option : 4

एक प्रतिष्ठित बहु-राष्ट्रीय कंपनी में एक निश्चित पद पर नियुक्ति के लिए निम्नलिखित योग्यताएँ आवश्यक हैं:

- A. अभ्यर्थी को 65% अंकों के साथ एमबीए अवश्य होना चाहिए।
- B. अभ्यर्थी ने न्यूनतम 50% अंकों के साथ चयन-परीक्षा अवश्य उत्तीर्ण की होनी चाहिए।
- C. अभ्यर्थी ने साक्षात्कार में न्यूनतम 65% अंक अवश्य प्राप्त किये हुए हों।
- D. अभ्यर्थी की आयु 1 सितंबर 2018 को 23 वर्ष से कम और 30 वर्ष से अधिक नहीं होनी चाहिए।

अभ्यर्थी के मामले में, जो अन्य सभी मानदंडों को पूरा करता है सिवाय:

- I. उपरोक्त (A) के, किंतु वह 50% अंक प्राप्तकर्ता इंजीनियर है, तो मामले को निदेशक, भर्ती के लिए संदर्भित किया जा सकता है।
- II. उपरोक्त (B) के, किंतु उसे कार्यकारी अधिकारी के रूप में कार्य करने का न्यूनतम 2 वर्षों का अनुभव है, तो मामले को सभापती, भर्ती समिति को संदर्भित किया जा सकता है।

नीचे एक अभ्यर्थी के संबंध में जानकारी दी गई है। उपरोक्त मानदंडों और शर्तों के संदर्भ में इसका विश्लेषण करें और फिर उचित कार्रवाई का निर्णय लें। आपको दी गई जानकारी के अतिरिक्त कुछ भी नहीं मानना है।
श्वेता शर्मा ने यांत्रिक अभियांत्रिकी (मैकेनिकल इंजीनियरिंग) पूर्ण करने के पश्चात् मुक्त-विद्यालय (ओपन स्कूल) के माध्यम से एमबीए किया। उसने एमबीए में 55% अंक और अभियांत्रिकी (इंजीनियरिंग) पाठ्यक्रम में 75% अंक प्राप्त किये। उसने चयन परीक्षा में 65% अंक और साक्षात्कार में 70% अंक प्राप्त किये। उसकी जन्म तिथि 25 दिसंबर 1992 है।

Ans 1.

यह मामला निदेशक, भर्ती को संदर्भित किया जाना है।

2. अभ्यर्थी का चयन किया जाना है।

3.

यह मामला सभापती, भर्ती समिति को संदर्भित किया जाना है।

4. अभ्यर्थी का चयन नहीं किया जाना है।

Q.3 In a code language, 'WORK' is written as 'XOSL' and 'TIME' is written as 'UINE'. How will 'SALARY' be written?

- Ans 1. TAMASY
 2. TAMASZ
 3. TAMBSZ
 4. TBMBSZ

Question ID : 1860452006
Status : Answered
Chosen Option : 2

Q.4 Eight friends P, Q, R, S, T, U, V and W are sitting around a circular table. U is on the immediate right of Q. V is the neighbour of T. R is between T and U. W is on the immediate left of P but is not the neighbour of T or S. What is the position of S?

- Ans 1. Between Q and U

Question ID : 1860452001
Status : Answered
Chosen Option : 2

- ☒ 2. On the immediate left of Q
- ☐ 3. On the immediate left of P
- ☐ 4. Second to the right of U

Q.5 दिये गए कथनों को सत्य मानें, भले ही वे तथ्यात्मक रूप से अर्थहीन हों, और निर्णय लें कि कौन सा/ कौन से निष्कर्ष तर्कसंगत रूप से कथनों का अनुसरण करता/करते है/हैं।

कथन:

सभी अधिकारी स्नातक हैं। सभी लिपिक स्नातक हैं।

निष्कर्ष:

I. कुछ स्नातक अधिकारी हैं।

II. सभी स्नातक अधिकारी हैं।

Ans

- ☒ 1. केवल निष्कर्ष I अनुसरण करता है।
- ☐ 2. निष्कर्ष I और निष्कर्ष II, दोनों ही अनुसरण करते हैं।
- ☐ 3. केवल निष्कर्ष II अनुसरण करता है।
- ☐ 4. न तो निष्कर्ष I और न ही निष्कर्ष II अनुसरण करते हैं।

Question ID : 1860452002

Status : Answered

Chosen Option : 1

Q.6 The equal number of houses on both sides of the street are numbered 1, 2, 3, 4...up one side, then back down the other side. If house number nine (9) is opposite house number 24, then how many houses are there on the street?

Ans

- ☐ 1. 36
- ☐ 2. 30
- ☒ 3. 32
- ☐ 4. 34

Question ID : 1860452004

Status : Answered

Chosen Option : 2

Q.7

Question ID : 1860452008

Status : Answered

Chosen Option : 1

एक प्रतिष्ठित बहु-राष्ट्रीय कंपनी में, एक निश्चित पद पर नियुक्ति के लिए निम्नलिखित योग्यताएँ आवश्यक हैं:

- A. अभ्यर्थी को न्यूनतम 65% अंकों के साथ एमबीए अवश्य होना चाहिए।
- B. अभ्यर्थी ने न्यूनतम 50% अंकों के साथ चयन-परीक्षा उत्तीर्ण अवश्य की होनी चाहिए।
- C. अभ्यर्थी ने साक्षात्कार में न्यूनतम 65% अंक अवश्य प्राप्त किये हुए हों।
- D. अभ्यर्थी की आयु 1 सितंबर 2018 को 23 वर्ष से कम और 30 वर्ष से अधिक नहीं होनी चाहिए।

अभ्यर्थी के मामले में जो अन्य सभी मानदंडों को पूरा करता है सिवाय:

- I. उपरोक्त (A) के, किंतु वह 50% अंक प्राप्तकर्ता इंजीनियर है, तो मामले को निदेशक, भर्ती के लिए संदर्भित किया जा सकता है।
- II. उपरोक्त (B) के, किंतु उसे कार्यकारी अधिकारी के रूप में कार्य करने का कम से कम 2 वर्ष का अनुभव है, तो मामले को सभापती, भर्ती समिति को संदर्भित किया जा सकता है।

नीचे एक अभ्यर्थी के संबंध में जानकारी दी गई है। उपरोक्त मानदंडों और शर्तों के संदर्भ में इसका विश्लेषण करें और फिर उचित कार्रवाई का निर्णय लें। आपको दी गई जानकारी के अतिरिक्त कुछ भी नहीं मानना है।

सोहेल सिंह 76% अंकों के साथ एमबीए है। वह दिसंबर 2016 से अपने चाचा की फ़र्म में एक कार्यकारी अधिकारी के रूप में कार्य कर रहा है। उसने चयन परीक्षा में 72% अंक और साक्षात्कार में 70% अंक प्राप्त किये हैं। उसकी जन्म तिथि 14 अगस्त 1993 है।

Ans

✓ 1. अभ्यर्थी का चयन किया जाना है।

✗ 2.

यह मामला सभापती, भर्ती समिति को संदर्भित किया जाना है।

✗ 3. अभ्यर्थी का चयन नहीं किया जाना है।

✗ 4.

यह मामला निदेशक, भर्ती को संदर्भित किया जाना है।

Q.8 In a class test of 45 students, one student is ranked 25th. What is his rank from the bottom?

Ans

✓ 1. 21st

✗ 2. 25th

✗ 3. 20th

✗ 4. 22nd

Question ID : 1860452005

Status : Answered

Chosen Option : 1

Q.9 Select the option that is related to the third term in the same way as the second term is related to the first term.

5 : 216 :: 7 : ?

Ans

✗ 1. 343

✗ 2. 196

Question ID : 1860451998

Status : Answered

Chosen Option : 4

- ✗ 3. 729
- ✓ 4. 512

Q.10 From the given alternatives select the word which CANNOT be formed using the letters of the given word.

APPRECIATE

- Ans
- ✗ 1. RECEIPT
 - ✗ 2. PRECEPT
 - ✓ 3. CREATOR
 - ✗ 4. APPEAR

Question ID : 1860452003
Status : Answered
Chosen Option : 3

Q.11 Select the number pair which is different from the other three responses.

- Ans
- ✗ 1. 19, 132
 - ✗ 2. 39, 272
 - ✗ 3. 31, 216
 - ✓ 4. 23, 161

Question ID : 1860452007
Status : Answered
Chosen Option : 4

Q.12 निम्नलिखित संख्या अनुक्रम में ऐसी कितनी सम संख्याएँ हैं जिनमें से प्रत्येक के तुरंत पश्चात् एक विषम संख्या और ठीक पहले एक सम संख्या है?


4 8 7 6 8 9 5 6 9 5 7 8 4 6 9 5 5 8 8 6 7 7 9

- Ans
- ✗ 1. एक
 - ✗ 2. दो
 - ✗ 3. तीन
 - ✓ 4. चार

Question ID : 1860452000
Status : Answered
Chosen Option : 4

Section : Circuit Analysis

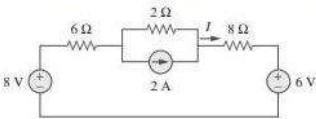Q.1 Calculate current I in the following circuit using super position theorem.



- Ans
- ✓ 1. 375 mA
 - ✗ 2. 200 mA
 - ✗ 3. 150 mA
 - ✗ 4. 100 mA

Question ID : 1860452033
Status : Answered
Chosen Option : 1

Q.2 A 230 V lamp is rated to pass a current of 0.24 A. Calculate its power output. If a second similar lamp is connected in parallel to the lamp, calculate the supply current required to give the same power output in each lamp.


- Ans
- ✗ 1. 0.24 A
 - ✗ 2. 1.5 A
 - ✗ 3. 1.9 A
 - ✓ 4. 0.48 A

Question ID : 1860452027
Status : Answered
Chosen Option : 4

Q.3

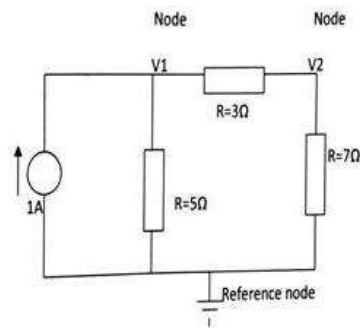Question ID : 1860452016
Status : Answered
Chosen Option : 2

The value of voltages V_1 and V_2 for the circuit shown below is:
(Use Nodal Analysis)



- Ans
- ☒ 1. $7/10$ V, $3/7$ V
 - ☒ 2. $10/3$ V, $7/3$ V
 - ☒ 3. $3/10$ V, $3/7$ V
 - ☒ 4. $1/7$ V, $3/4$ V

Q.4 If two capacitors having capacitances of $5\text{ }\mu\text{F}$ and $10\text{ }\mu\text{F}$ respectively are connected in series across a 200 V supply, find the potential difference across each capacitor.

- Ans
- ☒ 1. 50 V , 100 V
 - ☒ 2. 133.33 V , 66.66 V
 - ☒ 3. 200 V , 100 V
 - ☒ 4. 100 V , 200 V

Question ID : 1860452032

Status : Answered

Chosen Option : 2

Q.5 A heater takes a current of 7 A from a 230 V source for 12 h . Calculate the energy consumed (in kWh).


- Ans
- ☒ 1. 2.76 kWh
 - ☒ 2. 1.61 kWh
 - ☒ 3. 38.64 kWh
 - ☒ 4. 19.32 kWh

Question ID : 1860452028

Status : Answered

Chosen Option : 4

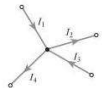Q.6 For the network junction shown in the figure, calculate the current I_3 , given that $I_1 = 3\text{ A}$, $I_2 = 4\text{ A}$ and $I_4 = 2\text{ A}$.




- Ans
- ☒ 1. 3 A
 - ☒ 2. 4 A
 - ☒ 3. 2 A
 - ☒ 4. 6 A

Question ID : 1860452026

Status : Answered

Chosen Option : 1

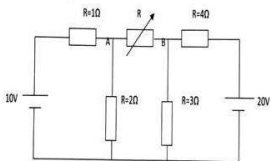Q.7 The value of R , for which the maximum power transferred across AB of the circuit shown in the figure below is:



- Ans
- ☒ 1. $23.8\text{ }\Omega$
 - ☒ 2. $238\text{ }\Omega$


Question ID : 1860452018

Status : Answered

Chosen Option : 3

- ✓ 3. $2.38\ \Omega$
✗ 4. $3\ \Omega$


Q.8 For the circuit shown in the figure, the value of current 'I' is ____.

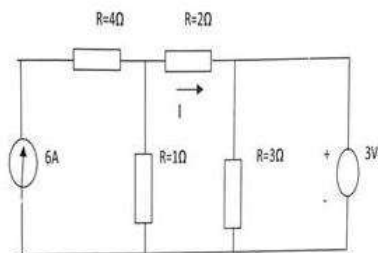

Question ID : 1860452019
Status : Answered
Chosen Option : 1

- Ans ✓ 1. 1 A
✗ 2. 2 A
✗ 3. 3 A
✗ 4. Zero


Q.9 For the figure shown below, the value of the supply voltage 'V' is ____.

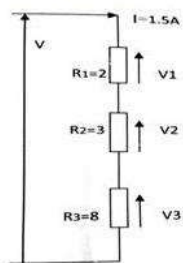

Question ID : 1860452010
Status : Answered
Chosen Option : 3

- Ans ✗ 1. 12 V
✗ 2. 4.5 V
✓ 3. 19.5 V
✗ 4. 3 V

Q.10 The value of currents in the network shown below is:

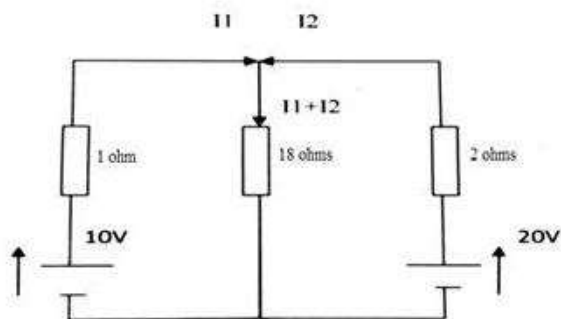

Question ID : 1860452015
Status : Answered
Chosen Option : 3

- Ans ✗ 1. 2.85 A, 3.57 A, 0.72 A
✗ 2. 2.85 A, -3.57 A, -0.72 A
✓ 3. -2.85 A, 3.57 A, 0.72 A

☒ 4. 2 A, 4 A, 6 A

Q.11 A conductor of 0.5 mm diameter wire has a resistance of 400 Ω . Find the resistance of the same length of wire if it's diameter were doubled.

- Ans** ☒ 1. 150 Ω
☒ 2. 50 Ω
☒ 3. 100 Ω
☒ 4. 200 Ω

Question ID : 1860452030

Status : Answered

Chosen Option : 3

Q.12 A resistance of 10 Ω is connected in series with two resistances, each of 15 Ω arranged in parallel. What resistance must be shunted across this parallel combination so that the total current taken shall be 1.5 A with 20 V applied voltage?


- Ans** ☒ 1. 8 Ω
☒ 2. 12 Ω
☒ 3. 5 Ω
☒ 4. 6 Ω

Question ID : 1860452024

Status : Answered

Chosen Option : 3

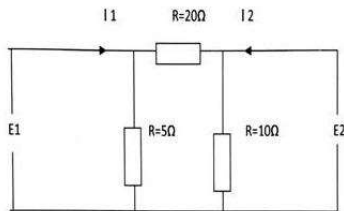Q.13 The value of admittance parameter Y_{12} for the two-port network shown in the figure is:




- Ans** ☒ 1. -0.05 mho
☒ 2. 0.1 mho
☒ 3. -0.2 mho
☒ 4. 0.05 mho

Question ID : 1860452020

Status : Answered

Chosen Option : 1

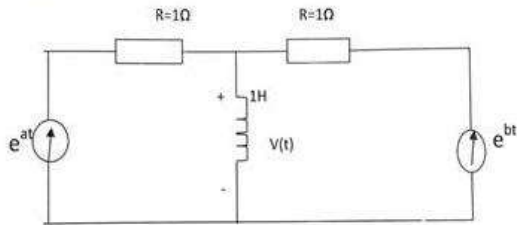Q.14 For the circuit shown in the figure, the value of voltage $v(t)$ is:




- Ans** ☒ 1. $ae^{at} + be^{bt}$
☒ 2. $e^{at} + e^{bt}$
☒ 3. $e^{at} - e^{bt}$
☒ 4. $ae^{at} - be^{bt}$

Question ID : 1860452022

Status : Answered

Chosen Option : 1

Q.15 For the network shown in the figure, calculate the effective resistance and the supply current.

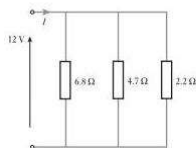


Question ID : 1860452025

Status : Answered

Chosen Option : 1

- Ans ☒ 1. 1.23 Ω , 9.76 A
☐ 2. 1.23 Ω , 4.88 A
☐ 3. 13.7 Ω , 4.88 A
☐ 4. 6.8 Ω , 9.76 A


Q.16 For the circuit shown in the figure, the value of voltage V_{AB} is _____.

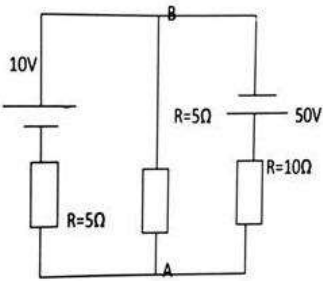

Question ID : 1860452021
Status : Answered
Chosen Option : 4

- Ans ☐ 1. 40 V
☐ 2. 25 V
☐ 3. 10 V
☒ 4. 6 V


Q.17 A voltage divider is to give an output voltage of 10 V from an input voltage of 30 V as shown in the figure. Given $R_2=100\ \Omega$. The value of resistance R_1 is:

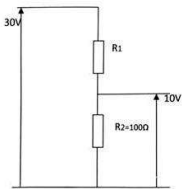

Question ID : 1860452011
Status : Answered
Chosen Option : 2

- Ans ☐ 1. 150 Ω
☒ 2. 200 Ω
☐ 3. 100 Ω
☐ 4. 300 Ω

Q.18 Find v_o in the following circuit using super position theorem.

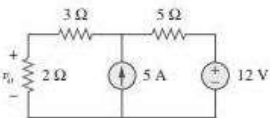


Question ID : 1860452031
Status : Answered
Chosen Option : 3

- Ans ☐ 1. 10 V
☐ 2. 12 V
☒ 3. 7.4 V
☐ 4. 4.6 V

Q.19

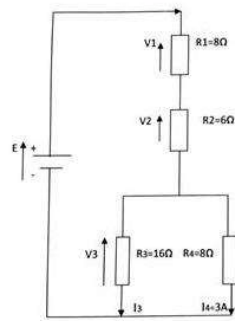
Question ID : 1860452014
Status : Answered
Chosen Option : 3

For the network shown in figure, the value of supply current and source emf is:



- Ans
- 1. 4.5 A, 36 V
 - 2. 1.5 A, 27 V
 - 3. 4.5 A, 87 V
 - 4. 1.5 A, 36 V

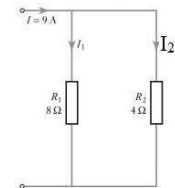Q.20 For the network shown in the figure, calculate the power developed by resistor R_1 and R_2 respectively.



- Ans
- 1. 160 W, 80 W
 - 2. 80 W, 160 W
 - 3. 140 W, 72 W
 - 4. 72 W, 140 W

Question ID : 1860452029

Status : Answered

Chosen Option : 4

Q.21 एक केबल में दो कंडक्टर हैं, जो कि परीक्षण के हेतुओं के लिए केबल के एक छोर पर इक साथ जोड़े गए हैं। जब केबल 700 m लम्बा हो, तब दूसरे छोर से नापने पर संयोजित लूप का रेसिस्टेंस 100 Ω पाया गया। 8 km लंबी समान केबल के रेसिस्टेंस का मूल्य _____ है।

- Ans
- 1. 1,100 Ω
 - 2. 1,134 Ω
 - 3. 1,200 Ω
 - 4. 1,143 Ω

Question ID : 1860452013

Status : Not Answered

Chosen Option : --

Q.22 A coil of resistance 20 Ω and inductance 10 mH is in series with a capacitance and is supplied with a constant voltage, variable frequency source. The maximum current is 2 A at 1000 Hz. The Q-factor of the circuit is ____.


- Ans
- 1. 31.8
 - 2. 3.14
 - 3. 314
 - 4. 31.4

Question ID : 1860452023

Status : Answered

Chosen Option : 2

Q.23 The value of potential difference across the 2 Ω resistor for the network shown below is:

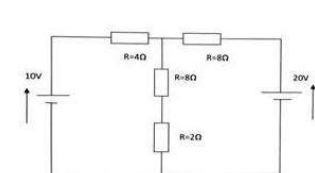


Question ID : 1860452017

Status : Answered

Chosen Option : 4

- Ans ☒ 1. 2.8 V
☒ 2. 10.1 V
☒ 3. 5.2 V
☒ 4. 2.1 V

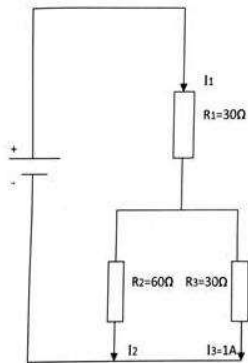Q.24 For the circuit shown in the figure below, the value of currents I_1 and I_2 is:



- Ans ☒ 1. 2.5 A, 1.5 A
☒ 2. 3 A, 2.5 A
☒ 3. 1 A, 1.5 A
☒ 4. 1.5 A, 0.5 A

Question ID : 1860452012
Status : Answered
Chosen Option : 4

Section : Machines

Q.1 A transformer has 400 W as iron loss at full load. The iron loss at half full load will be ____.

- Ans ☒ 1. 400 W
☒ 2. 800 W
☒ 3. 100 W
☒ 4. 200 W

Question ID : 1860452044
Status : Answered
Chosen Option : 1

Q.2 A two-pole alternator is running at 1,500 rpm. Its angular velocity will be ____.

- Ans ☒ 1. 192 rad/s
☒ 2. 157 rad/s
☒ 3. 212 rad/s
☒ 4. 118 rad/s

Question ID : 1860452053
Status : Answered
Chosen Option : 2

Q.3 In a split-phase induction motor, the two stator windings ____.

- Ans ☒ 1. have equal R/X_L ratio
☒ 2. draw only the in-phase currents
☒ 3. are mutually displaced by 90° electrically
☒ 4. draw equal currents

Question ID : 1860452052
Status : Answered
Chosen Option : 3

Q.4 Core lamination in a transformer decreases ____.

- Ans ☒ 1. eddy current loss
☒ 2. hysteresis loss

Question ID : 1860452041
Status : Answered
Chosen Option : 1

- ☒ 3. copper loss
- ☒ 4. leakage reactance

Q.5 A three-phase induction motor is running at 4% slip. If the input to the rotor is 1,000 W, then the mechanical power developed by the motor will be ____.

- Ans**
- ☒ 1. 960 W
 - ☒ 2. 9,600 W
 - ☒ 3. 96 W
 - ☒ 4. 0.96 W

Question ID : **1860452048**
Status : **Answered**
Chosen Option : **1**

Q.6 The armature of a DC machine is placed on the rotor to ____.

- Ans**
- ☒ 1. reduce losses
 - ☒ 2. save iron
 - ☒ 3. support commutation
 - ☒ 4. decrease armature reaction

Question ID : **1860452034**
Status : **Answered**
Chosen Option : **3**

Q.7 A washing machine generally employs a _____ motor.

- Ans**
- ☒ 1. shaded pole
 - ☒ 2. resistance split phase
 - ☒ 3. single-phase series
 - ☒ 4. hysteresis

Question ID : **1860452051**
Status : **Answered**
Chosen Option : **3**

Q.8 An open circuit test on a transformer gives ____.

- Ans**
- ☒ 1. friction losses
 - ☒ 2. iron losses
 - ☒ 3. total losses
 - ☒ 4. copper losses

Question ID : **1860452040**
Status : **Answered**
Chosen Option : **2**

Q.9 In a 6-pole DC machine, 90 mechanical degrees corresponds to how many electrical degrees?

- Ans**
- ☒ 1. 270
 - ☒ 2. 180
 - ☒ 3. 30
 - ☒ 4. 45

Question ID : **1860452057**
Status : **Answered**
Chosen Option : **1**

Q.10 A _____ motor runs at the highest speed when the load is removed.

- Ans**
- ☒ 1. cumulatively compound
 - ☒ 2. series
 - ☒ 3. shunt
 - ☒ 4. differentially compound

Question ID : **1860452037**
Status : **Answered**
Chosen Option : **2**

Q.11 The magnetic flux path in a transformer must have ____.

- Ans**
- ☒ 1. high resistance

Question ID : **1860452054**
Status : **Answered**

- ☒ 2. low resistance
- ☒ 3. high reluctance
- ☒ 4. low reluctance

Chosen Option : 4

Q.12 Leakage flux in a transformer ____.

- Ans
- ☒ 1. helps in the transfer of energy
 - ☒ 2. produces mutually-induced emf
 - ☒ 3. is minimised by interleaving the primary and secondary windings
 - ☒ 4. is negligible at full load

Question ID : 1860452042

Status : Answered

Chosen Option : 3

Q.13 The primary of a ____ should never be energised when its secondary is open circuited.

- Ans
- ☒ 1. potential transformer
 - ☒ 2. current transformer
 - ☒ 3. autotransformer
 - ☒ 4. power transformer

Question ID : 1860452043

Status : Answered

Chosen Option : 2

Q.14 For a simplex wave wound generator, emf generated path is given by ____.

Φ : Flux/ pole in Weber
Z : Total number of armature conductors
P : Number of generator poles
N : Armature rotation in revolution per minute (rpm)

- Ans
- ☒ 1. $(\phi PN)/120$
 - ☒ 2. $(\phi ZPN)/120$
 - ☒ 3. $(\phi ZPN)/180$
 - ☒ 4. $(\phi ZN)/60$

Question ID : 1860452056

Status : Answered

Chosen Option : 2

Q.15 Three-phase wound rotor motors are commonly called as ____ motors.

- Ans
- ☒ 1. Synchronous
 - ☒ 2. Commutator
 - ☒ 3. Slip ring
 - ☒ 4. Series

Question ID : 1860452047

Status : Answered

Chosen Option : 3

Q.16 Running the machine at no load is NOT recommended for a/an ____.

- Ans
- ☒ 1. induction motor
 - ☒ 2. DC shunt motor
 - ☒ 3. synchronous motor
 - ☒ 4. DC series motor

Question ID : 1860452038

Status : Answered

Chosen Option : 4

Q.17 ____ is a type of single-phase motor which has the lowest speed.

- Ans
- ☒ 1. Hysteresis
 - ☒ 2. Universal

Question ID : 1860452050

Status : Answered

Chosen Option : 3

- ☒ 3. Shaded pole
- ☒ 4. Repulsion

Q.18 A capacitor-start motor has a ____.

- Ans
- ☒ 1. high starting torque
 - ☒ 2. low efficiency
 - ☒ 3. low power factor
 - ☒ 4. high power factor

Question ID : 1860452049

Status : Answered

Chosen Option : 4

Q.19 The open-circuit characteristic of a DC generator is also called as ____ characteristics.

- Ans
- ☒ 1. internal
 - ☒ 2. performance
 - ☒ 3. external
 - ☒ 4. no load saturation

Question ID : 1860452035

Status : Answered

Chosen Option : 1

Q.20 The direction of rotation of field in a three-phase induction motor depends on the ____.

- Ans
- ☒ 1. supply voltage
 - ☒ 2. number of poles
 - ☒ 3. supply frequency
 - ☒ 4. phase sequence of supply voltage

Question ID : 1860452045

Status : Answered

Chosen Option : 4

Q.21 The function of dummy coils in DC machines is to ____.

- Ans
- ☒ 1. improve commutation
 - ☒ 2. reduce machine cost
 - ☒ 3. mechanically balance the armature
 - ☒ 4. increase efficiency

Question ID : 1860452036

Status : Answered

Chosen Option : 3

Q.22 To obtain greater efficiency, the slip of an induction motor should be ____.

- Ans
- ☒ 1. low
 - ☒ 2. very high
 - ☒ 3. high
 - ☒ 4. 1

Question ID : 1860452046

Status : Answered

Chosen Option : 1

Q.23 The current drawn by a 220 V DC motor of armature resistance 0.5 Ω and back emf 180 V is ____.

- Ans
- ☒ 1. 0.8 A
 - ☒ 2. 80 A
 - ☒ 3. 8 A
 - ☒ 4. 18 A

Question ID : 1860452039

Status : Answered

Chosen Option : 2

Q.24 The magnetic flux density on the surface of an iron face is 1.5 T, which is the typical saturation level value of ferromagnetic material. Find the force density on the iron face.

Ans

Question ID : 1860452055

Status : Not Answered

- ☒ 1. $0.59 \times 10^6 \text{ N/m}^2$
- ☒ 2. $0.89 \times 10^6 \text{ N/m}$
- ☒ 3. $0.59 \times 10^6 \text{ N/m}$
- ☒ 4. $0.89 \times 10^6 \text{ N/m}^2$

Chosen Option : --

Section : **Electronics**

Q.1 How many diodes are used to construct half wave, full wave and bridge rectifier circuits, respectively?

- Ans** ☒ 1. 2,1,4
- ☒ 2. 2,4,1
- ☒ 3. 4,1,2
- ☒ 4. 1,2,4

Question ID : **1860452073**

Status : **Answered**

Chosen Option : **4**

Q.2 If the resolution of a digital-to-analogue converter is approximately 0.4% of its full scale range, then it is a/an ____:

- Ans** ☒ 1. 16-bit converter
- ☒ 2. 10-bit converter
- ☒ 3. 8-bit converter
- ☒ 4. 12-bit converter

Question ID : **1860452064**

Status : **Answered**

Chosen Option : **3**

Q.3 The product of the two binary numbers 011 and 110 is:

- Ans** ☒ 1. 01110
- ☒ 2. 11001
- ☒ 3. 10010
- ☒ 4. 11100

Question ID : **1860452066**

Status : **Answered**

Chosen Option : **3**

Q.4 Among the following, which is a fixed frequency oscillator?

- Ans** ☒ 1. Crystal oscillator
- ☒ 2. Phase-shift oscillator
- ☒ 3. Hartley oscillator
- ☒ 4. Colpitt's oscillator

Question ID : **1860452063**

Status : **Answered**

Chosen Option : **1**

Q.5 The circuit which produces the best stabilisation of an operating point is ____.

- Ans** ☒ 1. base bias
- ☒ 2. collector feedback
- ☒ 3. emitter bias
- ☒ 4. voltage divider

Question ID : **1860452060**

Status : **Answered**

Chosen Option : **4**

Q.6 The output and input voltages of an emitter-follower have a phase difference of ____.

- Ans** ☒ 1. 0°
- ☒ 2. 270°
- ☒ 3. 90°
- ☒ 4. 180°

Question ID : **1860452062**

Status : **Answered**

Chosen Option : **1**

Q.7 A+AB gets simplified to:

- Ans
- ☐ 1. AB
 - ☐ 2. B
 - ☐ 3. A+B
 - ☒ 4. A

Question ID : 1860452068
Status : Answered
Chosen Option : 4

Q.8 In a certain transistor, the emitter current is 1.04 times the collector current. If the emitter current is 12 mA, calculate the base current.

- Ans
- ☒ 1. 462 μ A
 - ☐ 2. 11.538 mA
 - ☐ 3. 462 mA
 - ☐ 4. 11.538 μ A

Question ID : 1860452071
Status : Answered
Chosen Option : 1

Q.9 State the respective ripple factor and efficiency of a full wave rectifier.

- Ans
- ☐ 1. 0.40, 80%
 - ☐ 2. 1.21, 40.1 %
 - ☐ 3. 0.81, 48%
 - ☒ 4. 0.48, 81.2 %

Question ID : 1860452072
Status : Answered
Chosen Option : 4

Q.10 State the octal equivalent of hexa decimal number (B34)₁₆.

- Ans
- ☐ 1. (6454)₈
 - ☐ 2. (4564)₈
 - ☒ 3. (5464)₈
 - ☐ 4. (5645)₈

Question ID : 1860452074
Status : Answered
Chosen Option : 3

Q.11 Zener diodes are used as ____.

- Ans
- ☒ 1. voltage regulators
 - ☐ 2. amplifiers
 - ☐ 3. oscillators
 - ☐ 4. rectifiers

Question ID : 1860452059
Status : Answered
Chosen Option : 1

Q.12 State the correct condition for transistor to operate in cut-off region.

- Ans
- ☐ 1. Emitter base junction: forward bias
Collector base junction: forward bias
 - ☐ 2. Emitter base junction: reverse bias
Collector base junction: forward bias
 - ☐ 3. Emitter base junction: forward bias
Collector base junction: reverse bias
 - ☒ 4. Emitter base junction: reverse bias
Collector base junction: reverse bias

Question ID : 1860452070
Status : Answered
Chosen Option : 4

Q.13

Voltage regulation is given by:

V_{NL} : Voltage at no load

V_{FL} : Voltage at full load

- Ans
- ☒ 1. $((V_{NL} + V_{FL}) / (V_{NL})) * 100\%$
 - ☒ 2. $((V_{NL} - V_{FL}) / (V_{NL})) * 100\%$
 - ☒ 3. $((V_{NL} - V_{FL}) / (V_{FL})) * 100\%$
 - ☒ 4. $((V_{NL} + V_{FL}) / (V_{FL})) * 100\%$

Question ID : 1860452075
Status : Answered
Chosen Option : 2

Q.14 The charge carriers which have the greatest mobility are the ____.

- Ans
- ☒ 1. electrons
 - ☒ 2. positive ions
 - ☒ 3. holes
 - ☒ 4. negative ions

Question ID : 1860452058
Status : Answered
Chosen Option : 1

Q.15 The ideal value of CMRR is ____.

- Ans
- ☒ 1. $-\infty$
 - ☒ 2. 1
 - ☒ 3. 0
 - ☒ 4. ∞

Question ID : 1860452065
Status : Answered
Chosen Option : 4

Q.16 State the respective decimal equivalent and hexa decimal equivalent of $(65)_{16}$.

- Ans
- ☒ 1. 53, 35
 - ☒ 2. 46, 65
 - ☒ 3. 65, 46
 - ☒ 4. 35, 53

Question ID : 1860452069
Status : Answered
Chosen Option : 1

Q.17 The lower and upper cut-off frequencies are also called as ____ frequencies.

- Ans
- ☒ 1. half resonant
 - ☒ 2. half power
 - ☒ 3. resonant
 - ☒ 4. side band

Question ID : 1860452061
Status : Answered
Chosen Option : 4

Q.18 The binary equivalent of decimal 22 is:

- Ans
- ☒ 1. 10110
 - ☒ 2. 10001
 - ☒ 3. 11010
 - ☒ 4. 11111

Question ID : 1860452067
Status : Answered
Chosen Option : 1

Section : Measurement

Q.1 Electrostatic-type instruments are primarily used as:

Question ID : 1860452086

Status : **Answered**
Chosen Option : 3

- Ans
- ☒ 1. wattmeters
 - ☒ 2. ohmmeters
 - ☒ 3. voltmeters
 - ☒ 4. ammeters

Q.2 Integrating meters are used for the measurement of:

Question ID : 1860452079
Status : **Answered**
Chosen Option : 3

- Ans
- ☒ 1. current
 - ☒ 2. phase
 - ☒ 3. energy
 - ☒ 4. voltage

Q.3 To ensure safety, what should be the resistance of the earthing electrode?

Question ID : 1860452083
Status : **Answered**
Chosen Option : 2

- Ans
- ☒ 1. high
 - ☒ 2. low
 - ☒ 3. safety does not depend on resistance
 - ☒ 4. medium

Q.4 An electrodynamicometer type of instruments find its major use as:

Question ID : 1860452082
Status : **Answered**
Chosen Option : 1

- Ans
- ☒ 1. both, a standard instrument and a transfer instrument
 - ☒ 2. a transfer instrument only
 - ☒ 3. a standard instrument only
 - ☒ 4. a type of indicator instrument

Q.5 A 741 Op-Amp has:

Question ID : 1860452084
Status : **Answered**
Chosen Option : 1

- Ans
- ☒ 1. 8 pins
 - ☒ 2. 9 pins
 - ☒ 3. 7 pins
 - ☒ 4. 6 pins

Q.6 The number of basic SI units is:

Question ID : 1860452081
Status : **Answered**
Chosen Option : 4

- Ans
- ☒ 1. 6
 - ☒ 2. 5
 - ☒ 3. 4
 - ☒ 4. 7

Q.7 The material of wires used for making standard resistances is usually:

Question ID : 1860452085
Status : **Answered**
Chosen Option : 1

- Ans
- ☒ 1. magnanin
 - ☒ 2. phosphor bronze
 - ☒ 3. nichrome

☒ 4. copper

Q.8 Megger is essentially a:

- Ans ☒ 1. dynamometer
☒ 2. mega-ohmmeter
☒ 3. series-type ohmmeter
☒ 4. shunt-type ohmmeter

Question ID : 1860452076
Status : Answered
Chosen Option : 2

Q.9 Air friction damping is used in a/an ____ instrument.

- Ans ☒ 1. hot wire
☒ 2. induction
☒ 3. moving iron
☒ 4. moving coil

Question ID : 1860452080
Status : Answered
Chosen Option : 3

Q.10 The two-part tariff is used for ____ consumers.

- Ans ☒ 1. domestic
☒ 2. commercial
☒ 3. industrial
☒ 4. agricultural

Question ID : 1860452087
Status : Answered
Chosen Option : 1

Q.11 The ____ bridge is frequency sensitive.

- Ans ☒ 1. Wien
☒ 2. Anderson
☒ 3. Wheatstone
☒ 4. Maxwell

Question ID : 1860452078
Status : Answered
Chosen Option : 1

Q.12 Which bridge is used to measure the inductance of a high Q inductor?

- Ans ☒ 1. Anderson
☒ 2. Hay
☒ 3. Maxwell
☒ 4. Wien

Question ID : 1860452077
Status : Answered
Chosen Option : 2

Section : Control System

Q.1 Which of the following is correct for over-damped and under-damped system, respectively?

- Ans ☒ 1. $\xi = 0, \xi = -1$
☒ 2. $\xi > 1, 0 < \xi < 1$
☒ 3. $\xi > 1, \xi = 0$
☒ 4. $0 < \xi < 1, \xi = -1$

Question ID : 1860452093
Status : Answered
Chosen Option : 2

Q.2 Any physical system that does NOT automatically correct for variation in its output is a/an:

Question ID : 1860452088

Ans ☒ 1. open-loop system ☐ 2. closed-loop system ☐ 3. stable system ☐ 4. unstable system	Qp (1) (1).html# Status : Answered Chosen Option : 1
Q.3 Determine the stability of system: s^3+s^2+s+4 Ans ☐ 1. Absolutely stable ☐ 2. Critically stable ☒ 3. Unstable ☐ 4. Marginally stable	Question ID : 1860452092 Status : Answered Chosen Option : 3
Q.4 The phase shift of a second-order system with a transfer function $1/s^2$ is: Ans ☒ 1. 180° ☐ 2. 90° ☐ 3. -90° ☐ 4. -180°	Question ID : 1860452090 Status : Answered Chosen Option : 4
Q.5 The frequency at which the phase angle is 180° is called the ____ frequency. Ans ☐ 1. break ☐ 2. critical ☒ 3. phase cross-over ☐ 4. cut-off	Question ID : 1860452089 Status : Answered Chosen Option : 3
Q.6 Determine transfer function if the impulse response is e^{-2t}. Ans ☒ 1. $1/(s+2)$ ☐ 2. $1/(s-2)$ ☐ 3. $1/(s+2)^2$ ☐ 4. $1/(s-2)^2$	Question ID : 1860452091 Status : Answered Chosen Option : 1
Section : Material system	
Q.1 ____ is a material that is used to make cable sheaths. Ans ☐ 1. Aluminium ☐ 2. Copper ☒ 3. Lead ☐ 4. Cast iron	Question ID : 1860452094 Status : Answered Chosen Option : 3
Q.2 What is the coordination number of a body-centred cubic structure? Ans	Question ID : 1860452095 Status : Answered

- ✓ 1. 8
- ✗ 2. 4
- ✗ 3. 6
- ✗ 4. 12

Chosen Option : 3

Q.3 Which of the following is NOT an example of a semiconductor material?

- Ans
- ✗ 1. Silicon
 - ✓ 2. Copper
 - ✗ 3. Germanium
 - ✗ 4. Arsenic

Question ID : 1860452098

Status : Answered

Chosen Option : 2

Q.4 Which of the following is an example of a monoclinic system?

- Ans
- ✗ 1. SiO₂
 - ✗ 2. CaF₂
 - ✓ 3. FeSO₄
 - ✗ 4. NaCl

Question ID : 1860452096

Status : Answered

Chosen Option : 4

Q.5 What is the atomic packing factor for BCC and FCC, respectively?

- Ans
- ✗ 1. 0.52, 0.78
 - ✗ 2. 0.74, 0.68
 - ✗ 3. 0.52, 0.74
 - ✓ 4. 0.68, 0.74

Question ID : 1860452097

Status : Answered

Chosen Option : 4

Q.6 State the electronic configuration of Argon.

- Ans
- ✗ 1. 1s²2p²2p⁶3s²3p⁶
 - ✗ 2. 1s²2s²2s⁶3p²3p⁶
 - ✓ 3. 1s²2s²2p⁶3s²3p⁶
 - ✗ 4. 1s²2p²2p⁶3s²3s⁶

Question ID : 1860452099

Status : Answered

Chosen Option : 3

Section : Rest

Q.1 The maximum firing angle that can be obtained by a pure resistive trigger circuit used in phase control circuit is:

- Ans
- ✗ 1. 180°
 - ✓ 2. 90°
 - ✗ 3. 45°
 - ✗ 4. 135°

Question ID : 1860452102

Status : Answered

Chosen Option : 1

Q.2 Buchholz relay is a/an:

- Ans
- ✗ 1. oil temperature-actuated relay
 - ✓ 2. gas-actuated relay

Question ID : 1860452101

Status : Answered

Chosen Option : 2

- ☒ 3. current-actuated relay
- ☒ 4. oil-actuated relay

Q.3 HRC fuses provide the best protection against:

- Ans
- ☒ 1. sparking
 - ☒ 2. short circuit
 - ☒ 3. fire
 - ☒ 4. lightning

Question ID : 1860452100
Status : Answered
Chosen Option : 2

Q.4 _____ combined together are called stray losses.

- Ans
- ☒ 1. Frictional loss and copper loss
 - ☒ 2. Field copper loss and iron loss
 - ☒ 3. Iron and mechanical losses
 - ☒ 4. Copper and iron losses

Question ID : 1860452104
Status : Answered
Chosen Option : 3

Q.5 Two coils in differential connection have self-inductance of 2 mH and 4 mH and a mutual inductance of 0.15 mH. The equivalent inductance of the combination will be:

- Ans
- ☒ 1. 5.9 mH
 - ☒ 2. 6.5 mH
 - ☒ 3. 5.7 mH
 - ☒ 4. 7 mH

Question ID : 1860452103
Status : Answered
Chosen Option : 3

Q.6 When the gain margin is positive and phase margin is negative, the system is:

- Ans
- ☒ 1. unstable
 - ☒ 2. highly stable
 - ☒ 3. oscillatory
 - ☒ 4. stable

Question ID : 1860452105
Status : Answered
Chosen Option : 1